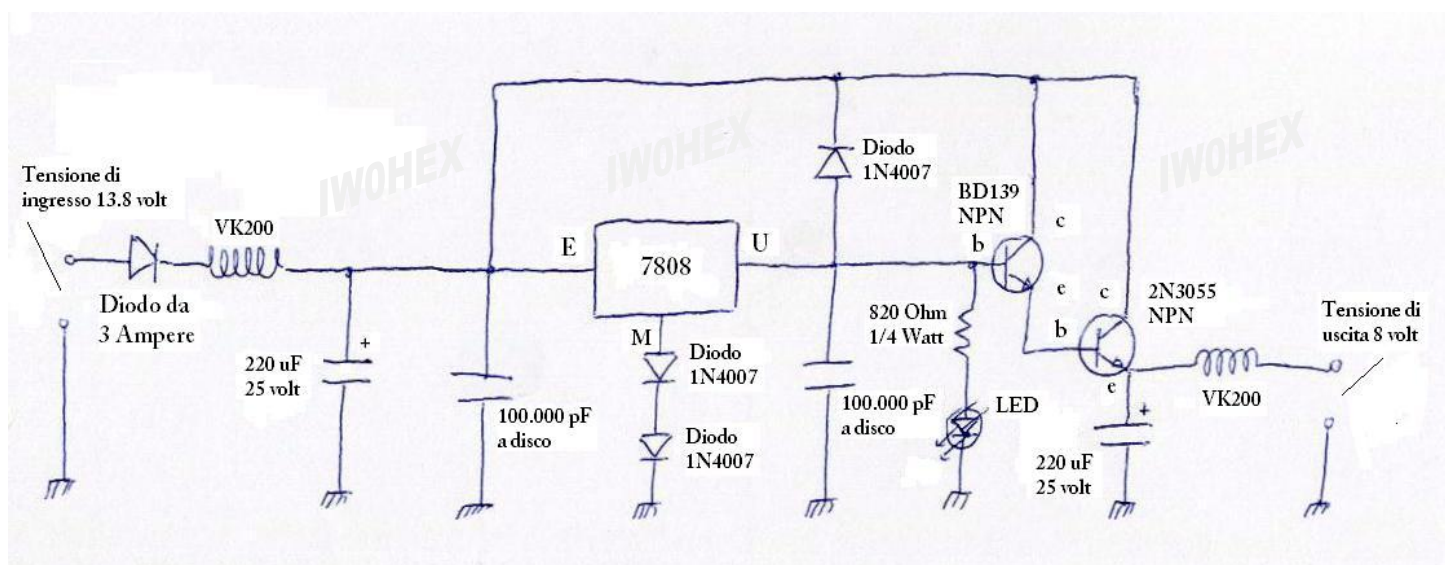


## Adapter power supply for IC-E90

I use this circuit on my IC-E90 and it's working very well.  
It's very easy to make. Low expensive, less than 10 €!!!



# IWOHEX